

## Ohm's Law BLM 3-21

Answer the following questions:

1. What is the resistance of a toaster if a current of 12.5 A flows through it when it is connected to 120 V?

---

2. A light bulb has a resistance of  $90\ \Omega$ . What current flows through the bulb when it is connected to 120 V?

---

3. A current of 0.50 A flows through a light bulb that has a resistance of  $18\ \Omega$ . What is the voltage across this light bulb?

---

4. A flashlight bulb has a resistance of  $4.0\ \Omega$ . What current passes through the bulb if it is connected to 3.0 V?

---

5. What potential difference is necessary to produce a current of 0.60 A in a load that has a resistance of  $25\ \Omega$ ?

---

6. The current through a load in a circuit is 2.5 A. If the potential difference across the load is 75 V, what is the resistance of the load?

---

7. (a) An 80 V potential difference is measured across a light bulb that has a resistance of  $16\ \Omega$ . What is the current through this light bulb?

---

(b) If the light bulb was replaced by a bulb with twice the resistance, what would be the new current through the bulb?

---

8. A 25 mA current flows through a  $300\ \Omega$  lamp. What is the voltage across the lamp?

---

